



EE5314 Class Notes

Hardware Guide

Spring 2011

Dr. Jason Losh

Basic Components

- 100mil (0.1”) square grid PCB with solder donuts
- 28p machine pin 300mil DIP socket
- Reset resistors and capacitor
- Voltage core capacitor
- Ceramic resonator (alt: crystal or TTL clock)
- User interface (push button, LED, ...)
- Power supply (batteries, ext supply, ICD3)
- Power supply filtering and bypass



Suggested Tools

- Soldering iron (30W or less) with small tip (chisel or needle point) properly tinned
- Solder (can contain lead, so be cautious)
- Cleaning device for solder tip
- Solder wick (for unsoldering)
- Diagonal cutter (watch for flying wires)
- Wire strippers
- Needle-nose pliers (for forming wires)
- Safety goggles! (for flying solder and wires)

Why Solder a Board?

- White breadboards
 - Connections are often intermittent
 - Ceramic resonators and crystal are problematic due to stray capacitance
 - Large pins will spring contacts
 - Larger current devices will have to be off-boarded
- Wire wrapping
 - Ceramic resonators and crystal are problematic due to extra lead inductance
 - Many devices under control exceed the current rating of 30ga wire (off-board issue above)

Basic Layout

- Start by arranging the parts with respect to the controller pins to minimize wiring runs
- Ceramic resonator should be very close to pins 8, 9, and 10
- Reset circuit should be by pin 1
- ICD3 connector should be by pin 1 and a PGECx/PGEDx pair
- Power supply bypassing by power pins

Power Distribution

- Our boards do not have a ground plane, so particular attention needs to be paid to power routing
- Point to point wiring can be very problematic, especially if transient high current devices are in the chain
- Try to star-wire (bring back ground and rail separately back to supply) to minimize source impedance
- Use storage caps for high current devices
- Use bypass caps on power pins of all devices
- Handle over-current, over-voltage correctly with TVS (transient voltage protection), fuse, PTC

Bypass Capacitance

- It is suggested that a $0.1\ \mu\text{F}$ surface mount or $0.01\ \mu\text{F}$ radial leaded ceramic cap should be placed close to the power pins of every device in the circuit (note: SMD has a lower ESL than a leaded capacitor)
- A $0.01\ \mu\text{F}$ radial leaded cap is approximated by a series RLC circuit with an ESL of $6\ \text{nH}$ (not including DIP pin) and an ESR of $0.2\ \Omega$, which is resonant at $\sim 20\ \text{MHz}$
- A bypass cap allows high-frequency currents to be supplied quickly to the local device and effectively lowers the series inductance of the supply to the device
- In other words, the short-term transient needs of the device are supplied by the capacitor and when the event is over, the capacitor is re-charged by the power supply
- The value of the capacitor is large function of the ground planes, capacitor packaging (SMD v. leaded), total number of decoupling caps and many other factors

Storage Capacitance


- Many devices, like memories, have large inrush currents at power up or when enabled
- This can create power “brown-outs” or transients on the board due to source or wiring impedances
 - This can lead to incomplete processor resets, raised noise floor in analog circuits like the A/D
- Larger caps (25-500 μF) act as a energy storage device, which effectively lowers the source impedance of the power supply at lower frequencies
- A 10 μF , low ESR capacitor is needed from V_{core} to V_{ss} for the processor core regulator

Π Filters

- A parallel C, series L, parallel C circuit is useful in creating a high-current low pass filter for noisy loads
- Some examples of noisy loads are switching capacitor and switched inductor power supplies, motors, and solenoids

Reset Circuit

 - Integrator consisting of a current source, R, and the storage device C
- When the circuit is de-energized, Vdd will be at 0V and the cap will discharge through R
- On power-up, R will charge C pulling \sim MCLR high after some time
- R1 limits current from C into the pin
- $R = 10\text{kohms}$, $C = 0.1\mu\text{F}$, $R1 = 10\text{ohms}$




Clock Sources

- Internal RC clock circuit (not accurate)
- External crystal or ceramic resonator used in a parallel resonant oscillator (on silicon)
 - XT mode (3-10 MHz)
 - HS mode (10-40 MHz)
- External clock source (EC mode)
- External crystal used by the secondary oscillator
 - Normally uses a 32.768 kHz oscillator used for the real-time clock

Phase-locked Loop

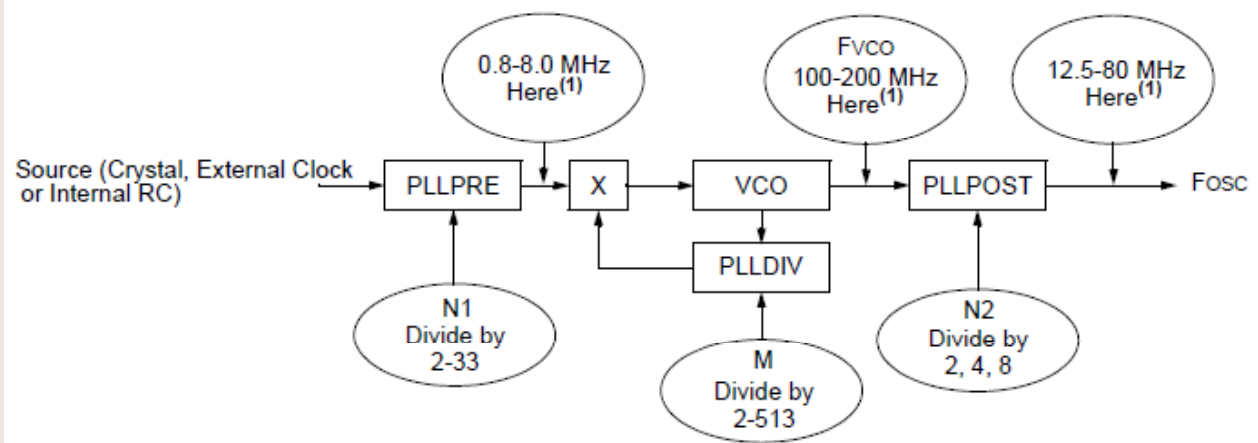- Used in XT, HS, and EC modes to allow a lower frequency resonator or clock source to be used
- Clock is prescaled ($\div 2$ to $\div 33$) to 0.8 to 8 MHz
- Voltage-controlled oscillator (VCO) output between 100-200 MHz is maintained at $2\times$ to $513\times$ by the PLL



Phase-locked Loop


- Output of VCO is post-scaled ($\div 2$, $\div 4$, or $\div 8$)
- Our designs use a final clock of 80 MHz and an 8 MHz ceramic resonator (XT mode)
- Important VCO Limitations
 - The VCO design only allows for a 100-200 MHz output
 - With power-on defaults of $\div 2$ pre-scale, x50 VCO/PLL, $\div 4$, the frequency input from the external clock or primary oscillator is bounded by 4 MHz and 8 MHz due
 - If outside this range, start the chip using the internal RC oscillator, reconfig the PLL, and switch to pri osc

Crystals

- Constructed from thin slabs of quartz (or similar material) sandwiched between two metal plates (electrodes)
- Simplest model (ignoring mechanical overtones) is a series RLC circuit (the motivational arm of the crystalline material) in parallel with a shunt capacitance C_s (due to the electrodes and the contained dielectric)
 - Looks like a 3-10 pF capacitor when not resonant (negative reactance)
 - Reactance is positive (inductive) when crystal is anti-resonant and real when crystal is series-resonant

Crystals

 
- For a typical crystals (1-20 MHz)
 - $L = 1\text{-}500\text{ mH}$, $C = .01\text{-.}03\text{ pF}$,
 $R = 10\text{-}100\ \Omega$, $C_s = 3\text{-}7\text{ pF}$
- Impedance:
 - $Z = (j\omega L + R + 1/j\omega C) // (1/j\omega(C_s + C_L))$
where C_L is the load of the stray capacitance,
oscillator circuit loading,
and discrete capacitors
across the crystal




Crystal Resonance

- Series resonance (where L and C are in resonance):
 - $f_S = [2 \times \pi \times (LC)^{1/2}]^{-1}$
 - $Z = R \parallel XC_S \rightarrow R$ ($X \rightarrow 0$) at f_S
- Anti-resonance (resonance of RLC in parallel with C_S and C_L (load)):
 - $f_A = [2\pi (LC (C_L + C_S)/(C + C_L + C_S))^{1/2}]^{-1}$
 - X is positive from f_S to f_A

Crystal Reactance

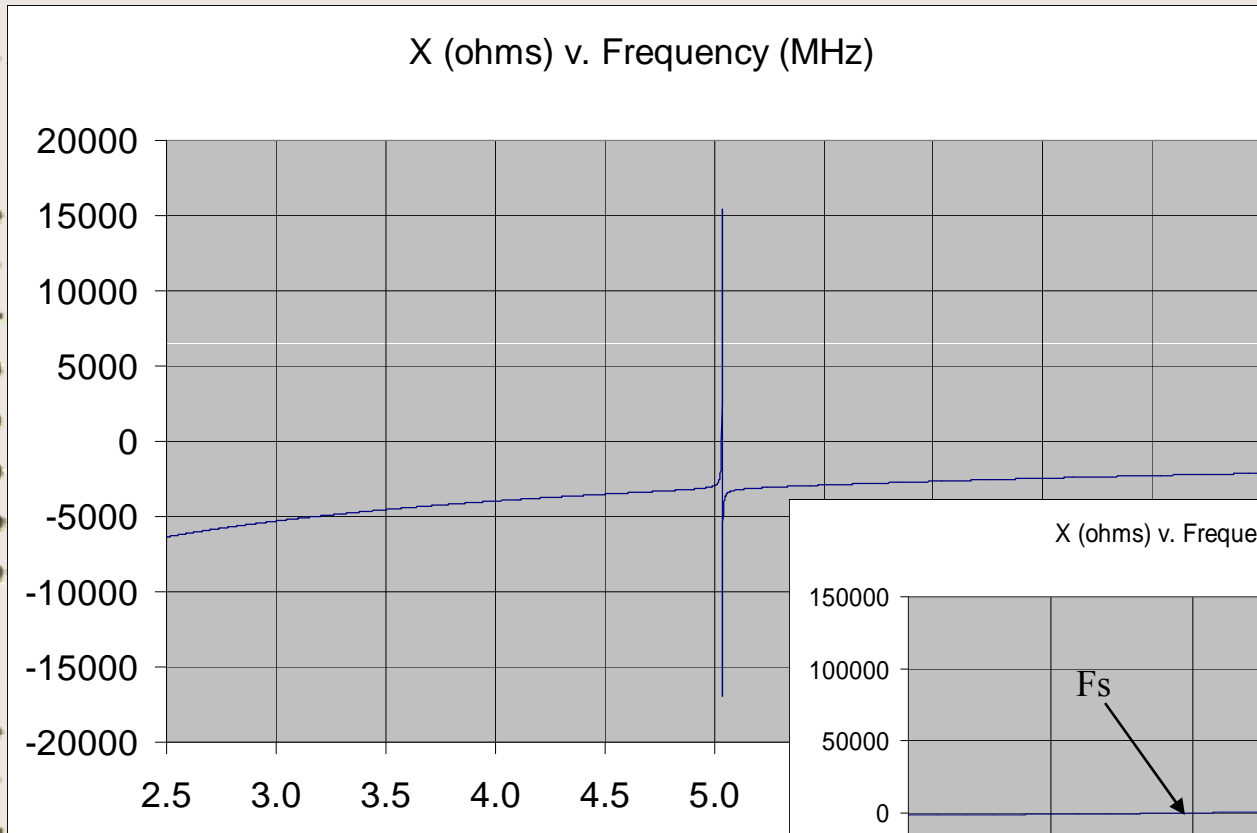

 - $R = 35 \Omega$
- $L = 100 \text{ mH}$
- $C = 0.01 \text{ pF}$
- $C_L + C_0 = 10 \text{ pF}$
- $F_s = 5.033 \text{ MHz}$




Oscillation

- Barkhausen Stability Criteria
 - Total phase shift around loop must be $N * 360^\circ$, where N is an integer
 - Closed loop gain must be greater than or equal to 1
- CMOS inverters are often used as the active device in oscillator circuits
 - Series resonating oscillators have two inverters and a crystal in the feedback term
 - Parallel resonating oscillators have one inverter and a crystal in the feedback term
(the primary oscillator in the PIC OSC1/2 pins)



Series Resonant Oscillator

 - Phase delay of the two inverters is $2 \times \tau_p \times f_{osc} \times 360^\circ$
- Crystal operating in the series resonant point give 0° of phase shift, so oscillator should work
- Problem: There is no way to accurately set the oscillation frequency and the circuit can oscillate at a non-resonant frequencies



Parallel Resonant Oscillator

  - One inverter gives a $\tau_p \times f_{osc} \times 360^\circ$ phase shift
- A phase shift network consisting of two parallel capacitors and a series inductor is used in the feedback path
- Between f_S and f_A the crystal reactance is positive (inductor)
- The exact frequency can be tweaked by varying the shunt C values
- This is the commonly used implementation



Ceramic Resonators


- Made of piezoelectric materials, like lead zirconate titanate (PZT)
- Lower cost alternative to crystals
- Less frequency accuracy than crystals
- Lower Q than crystals
- Can generally be used in the crystal circuits, with small modifications to the shunt capacitance to accommodate different resonator parameters

Clock Oscillator

- Crystal, parallel resonant oscillator, and logic-compatible driver
- Common clock oscillators are in metal hermetically-sealed package with 4 pins (power, ground, and output present)
- Lower part count, but higher cost
- The output is connected to OSC1 and the OSC2 pin can be used for general I/O


ICD3 Pinout

 - Pin 1 \sim MCLR
- Pin 2 Vdd
- Pin 3 Vss
- Pin 4 PGED_x
- Pin 5 PGEC_x
- Pin 6 N.C.



ICD3 Mechanics

RJ-12 Jack Top View

 

MPLAB Project Setup

- Project>New
Name the project and select a path, click OK
- Project>Select Language Toolsuite
Ensure MPLAB ASM30 Toolsuite is selected
(use MPLAB C30 Toolsuite for C code)
- View>Project
- Create ASM or C file (or use one from class) and save file at the path above
- In project toolbar, right click on Source Files to add the file above
- In project toolbar, right click on Linker Script to add the file “p33fj128mc802.gld” from the following location:
C:\Program Files\Microchip\MPLAB ASM30 Suite\Support\dsPIC33F\gld

MPLAB Settings for H/W Target

- Configure>Select Device: select 33FJ128MC802 device
- Configure>Configuration Bits set as appropriate for your hardware
- Typical deviations from the default configuration bit settings for 8 MHz ceramic resonator:
 - IESO is Start-up device with user-selected oscillator
 - FNOSC is Primary oscillator with PLL
 - POSCMS is XT Crystal Oscillator mode
 - FWDTEN is Watchdog timer enabled/disables by user
 - ICS as appropriate

Programming

- Programmer>Select Programmer>ICD3
- If your circuit needs only +3.3V and < 100 mA, then you can power the target hardware from the ICD3 checking the box
Programmer>Settings...>Power>Power target circuit from ICD3
- Programmer>Program
- Your hardware should be running